



North South University

<u>Course</u>	<u>CSE-231</u>
<u>Gropup</u>	<u>5</u>
<u>Submitted to</u>	<u>Dr Mohammad Monirujjaman Khan</u>
<u>Date</u>	<u>10-05-2021</u>

Submitted by:

<u>Name</u>	<u>Id</u>
<u>Istiak Ahmed Sheam</u>	<u>1911139642</u>
<u>Md Saeem Hossain Shanto</u>	<u>1912218642</u>
<u>Nur Kalam Mahin</u>	<u>1912254642</u>
<u>Farzana Haque</u>	<u>1821386042</u>

Our project was to show (EEE-2111) in seven segment display with the help of 555 timer. To complete this project, we have divided our work into two part.

1. Combinational Circuit Part
2. Sequential Circuit Part

Combinational Circuit Part:

We have 7 items to display. If we take 3 bit input, then we can display total $2^3=8$ outputs. So, to display (EEE-211), we can use 3 bit input.

First we have to draw the truth table with 3 bit input and expected output(output in seven segment display). Then for equations, we will k-map.

Combinational Circuit Making Process:

Truth Table:

Output in 7 segment display	A	B	C	a	b	c	d	e	f	g
E	0	0	0	1	0	0	1	1	1	1
E	0	0	1	1	0	0	1	1	1	1
E	0	1	0	1	0	0	1	1	1	1
-	0	1	1	0	0	0	0	0	0	1
2	1	0	0	1	1	0	1	1	0	1
1	1	0	1	0	1	1	0	0	0	0
1	1	1	0	0	1	1	0	0	0	0
X	1	1	1	X	X	X	X	X	X	X

K-Map:(SOP)

For – a:

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	1	0	x	0

$$a = A'C' + A'B' + B'C'$$

For – b:

A \ BC	0 0	0 1	1 1	1 0
0	0	0	0	0
1	1	1	x	1

$$b = A$$

For – c:

A \ BC	0 0	0 1	1 1	1 0
0	0	0	0	0
1	0	1	x	1

$$c = AC + AB$$

For - d :

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	1	0	x	0

$$d = A'C' + A'B' + B'C'$$

For - e :

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	1	0	x	0

$$e = B'C' + A'C' + A'B'$$

For - f :

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	0	0	x	0


$$f = A'B' + A'C'$$

For - g :

A \ BC	0 0	0 1	1 1	1 0
0	1	1	1	1
1	1	0	x	0

$$g = A' + B'C'$$

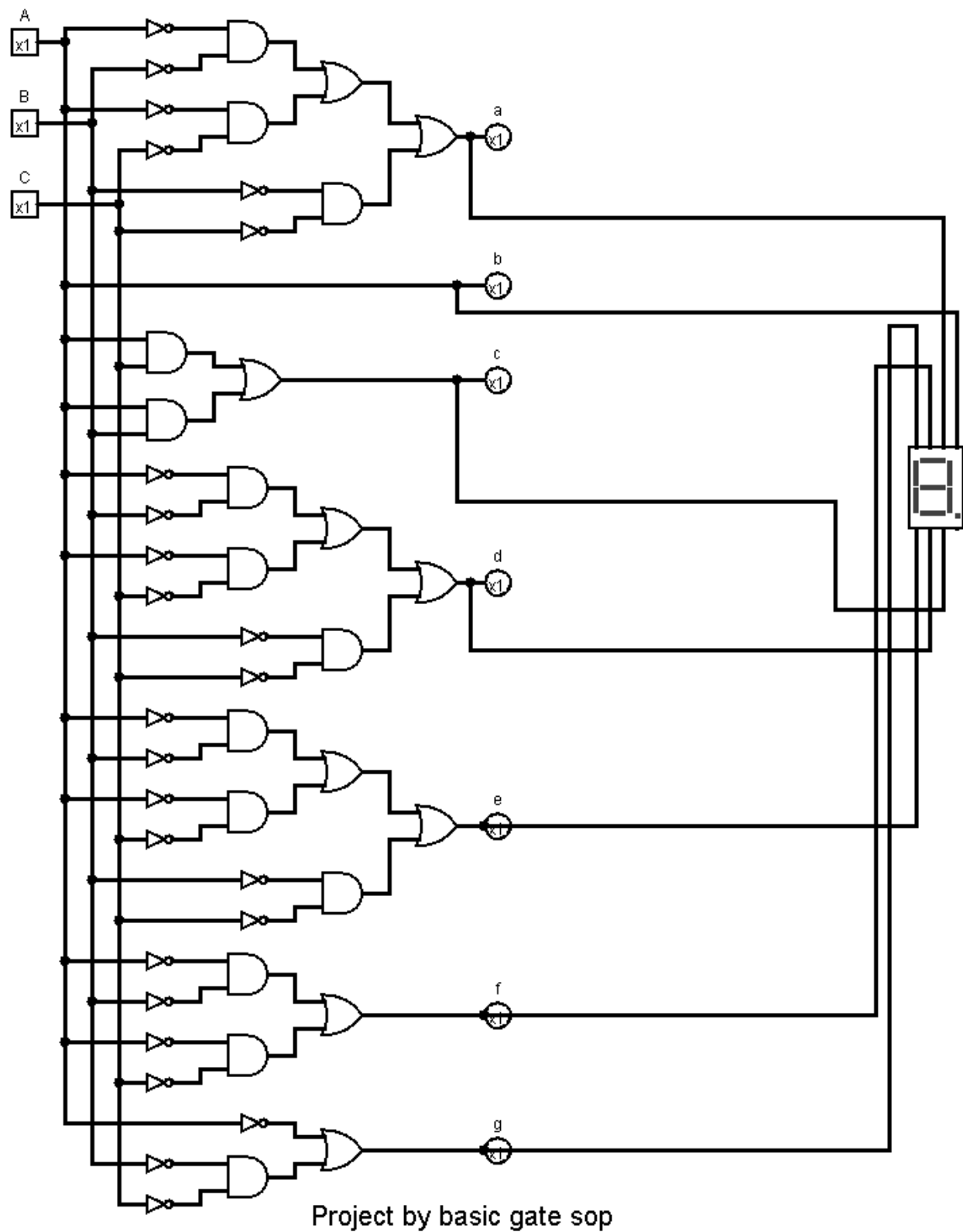Combinational Circuit for (EEE-211) by SOP:



K-Map:(POS)

For – a:

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	1	0	x	0

$$a = (B' + C')(A' + C')(A' + B')$$

For – b:

A \ BC	0 0	0 1	1 1	1 0
0	0	0	0	0
1	1	1	x	1

$$b = A$$

For – c:

A \ BC	0 0	0 1	1 1	1 0
0	0	0	0	0
1	0	1	x	1

$$c = A(B + C)$$

For - d:

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	1	0	x	0

$$d = (B' + C')(A' + C')(A' + B')$$

For - e :

Nbn

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	1	0	x	0

$$e = (B' + C')(A' + C')(A' + B')$$

For - f :

A \ BC	0 0	0 1	1 1	1 0
0	1	1	0	1
1	0	0	x	0


$$f = A'(B' + C')$$

For - g :

A \ BC	0 0	0 1	1 1	1 0
0	1	1	1	1
1	1	0	x	0

$$g = (A' + C')(A' + B')$$

 Combinational Circuit for (EEE-211) by POS:



project by POS

Sequential Circuit Part:

Sequential circuit will produce our continuous input with the help of 555 timer. For sequential part we are going to use **Synchronous Counter by T-FlipFlop**.

Required Equipment:

555 Timer IC:

The **555 timer IC** is an **integrated circuit (chip)** used in a variety of **timer**, delay, pulse generation, and oscillator applications.


T-FlipFlop:

Toggle Flip-flops are sequential logic circuits frequently used as single bit bistable storage elements in counters, memory devices or as frequency dividers in response to a clock pulse

Sequential Circuit Making Process:

We have used 3 bit input for combinational circuit. Now to produce that 3 bit continuous input we are going to use **3 bit synchronous counter**.

Loop for synchronous counter:

 

Excitation Table for T-FlipFlop:

Q	Output	T
0	0	0
0	1	1
1	0	1
1	1	0

State Table:

Output in 7 segment display	Decimal number	Present state			Next State			Next State Decoder		
		Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀	T ₂	T ₁	T ₀
E	0	0	0	0	0	0	1	0	0	1
E	1	0	0	1	0	1	0	0	1	1
E	2	0	1	0	0	1	1	0	0	1
-	3	0	1	1	1	0	0	1	1	1
2	4	1	0	0	1	0	1	0	0	1
1	5	1	0	1	1	1	0	0	1	1
1	6	1	1	0	<u>0</u>	<u>0</u>	<u>0</u>	1	1	0
	7	1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

K-map for T2:

Q ₂ \ Q ₁ Q ₀	0 0	0 1	1 1	1 0
0	0	0	1	0
1	0	0	1	1

$$T2 = Q1Q0 + Q2Q1$$

K-map for T1:

Q2 \ Q1Q0	0 0	0 1	1 1	1 0
0	0	1	1	0
1	0	1	1	1

$$T1 = Q0 + Q2Q1$$

K-map for T0:


Q2 \ Q1Q0	0 0	0 1	1 1	1 0
0	1	1	1	1
1	1	1	1	0

$$T0 = Q0 + Q1' + Q2'Q0'$$

$$= Q0 + Q1' + Q2$$


Logic Design for Sequential Circuit in Logisim:

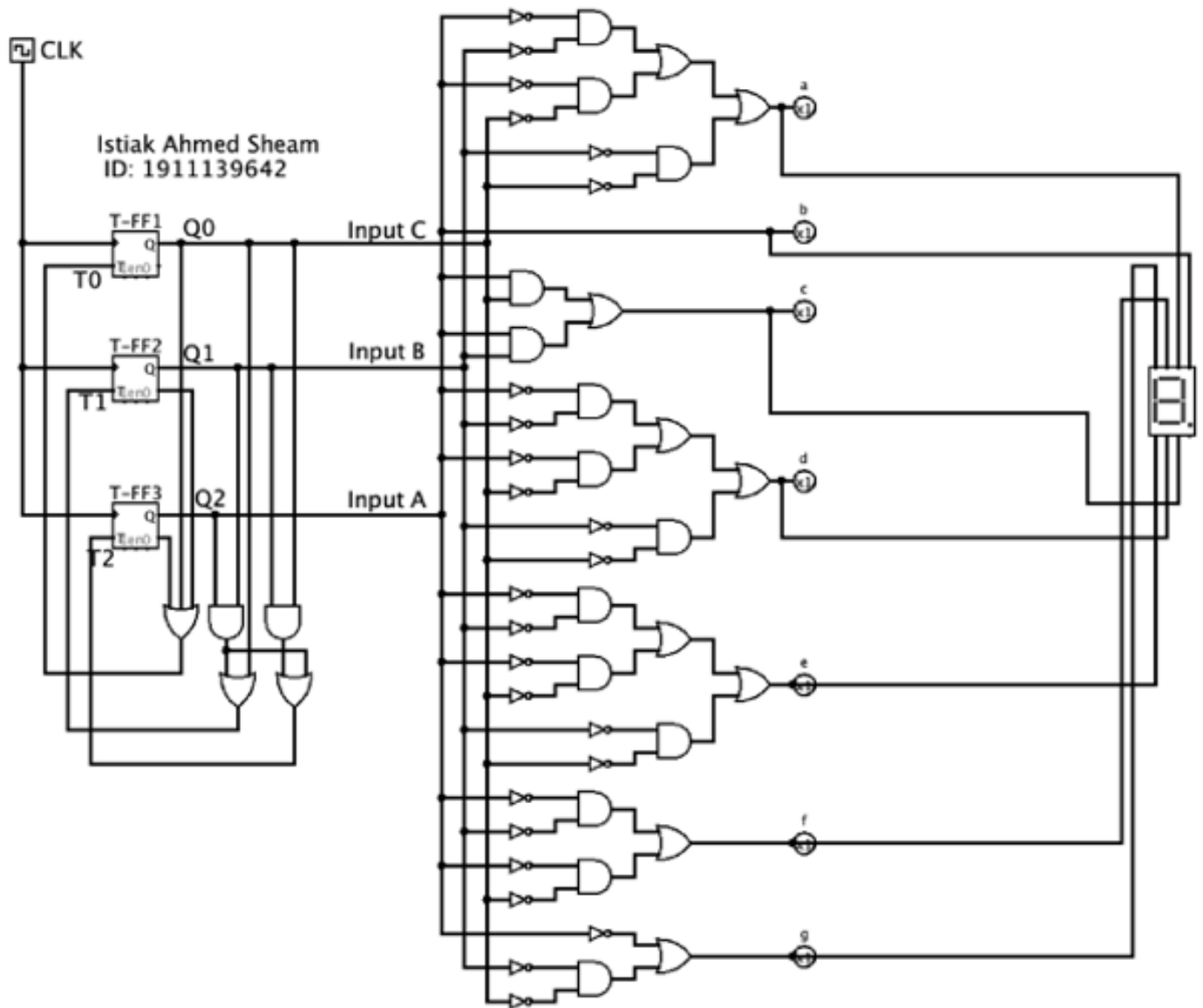To design this we need 555 Timer IC. But in logisim, we don't have 555 Timer IC. But we can use clock pulse in logisim instate of them.




displaying EEE-211 by synchronous counter input

Screenshots:

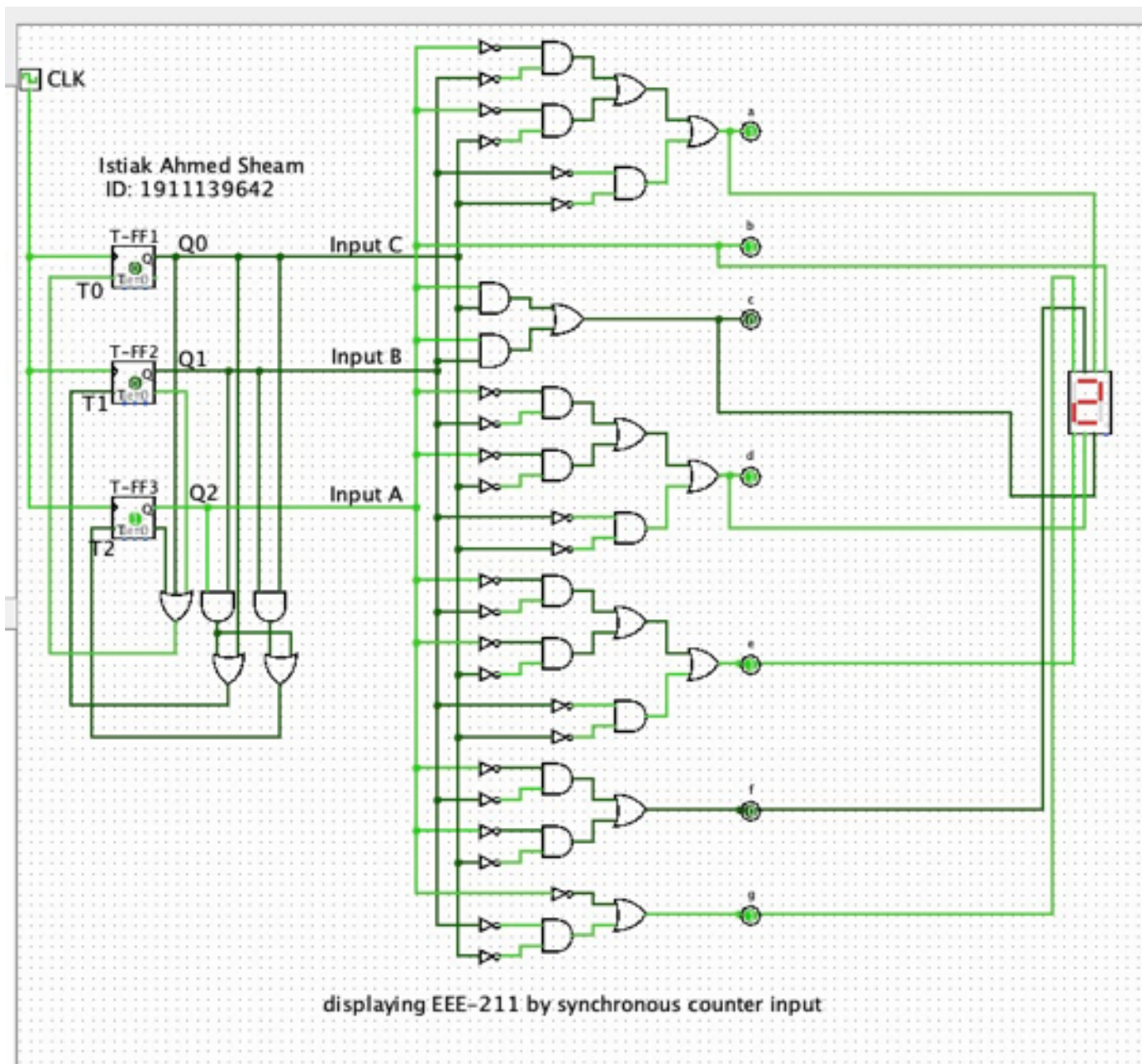


Isitak Ahmed Sheam 1911139642

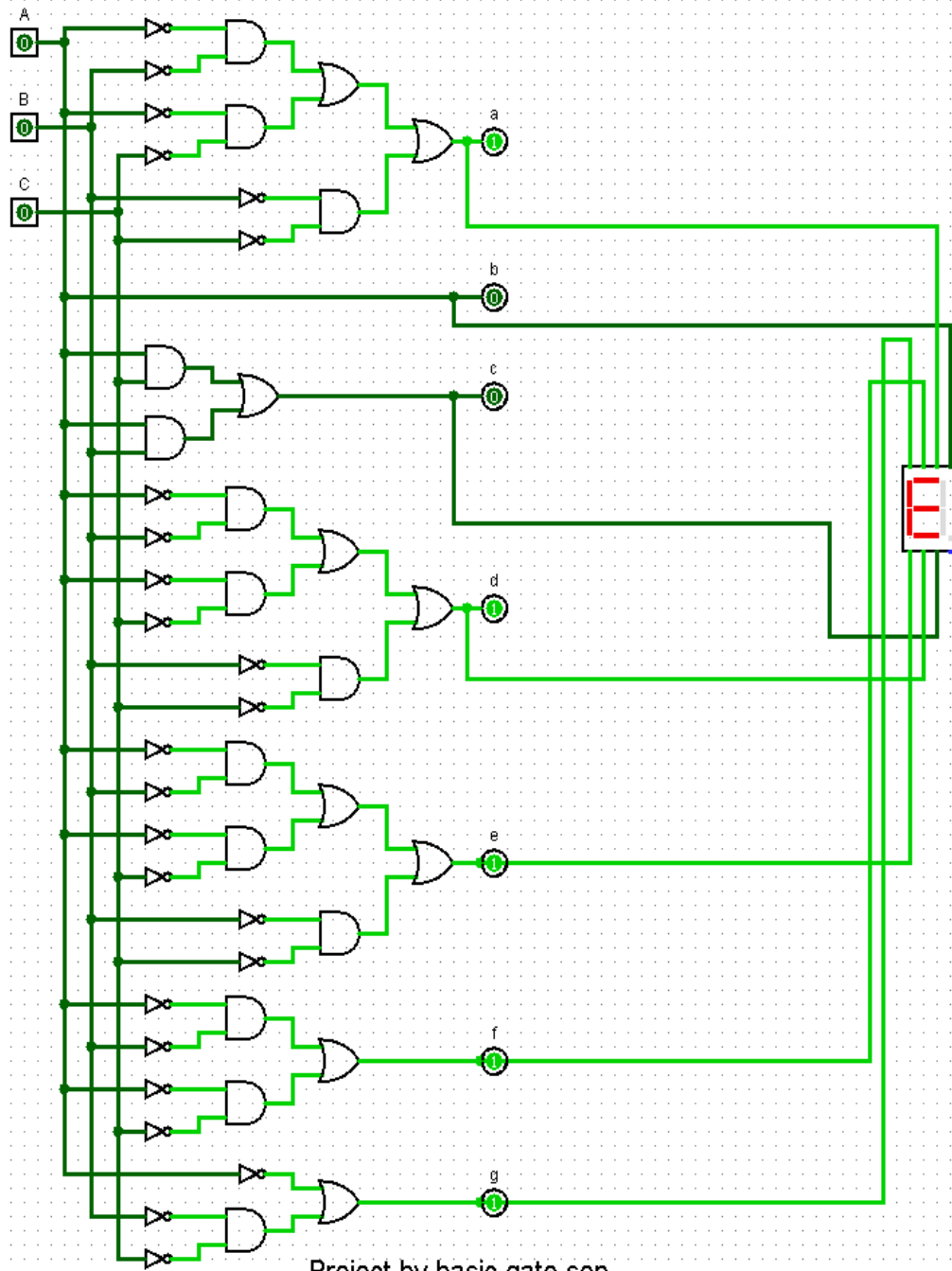

Project by basic gate sop


Md Saeem Hossain Shanto

1912218642

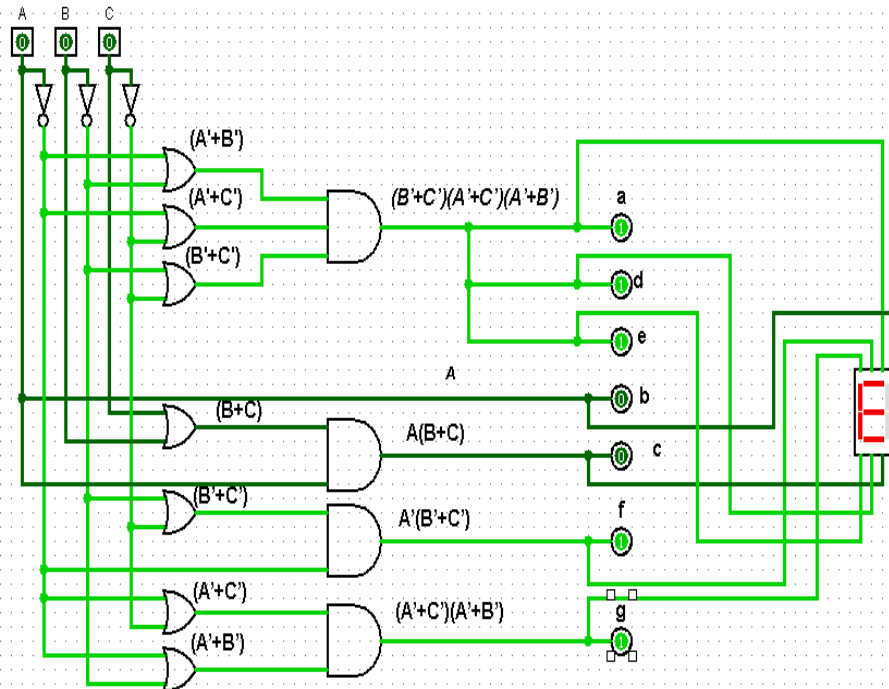


POS Circuit implementation with basic gates

Nur Kalam Mahin (1912254642)

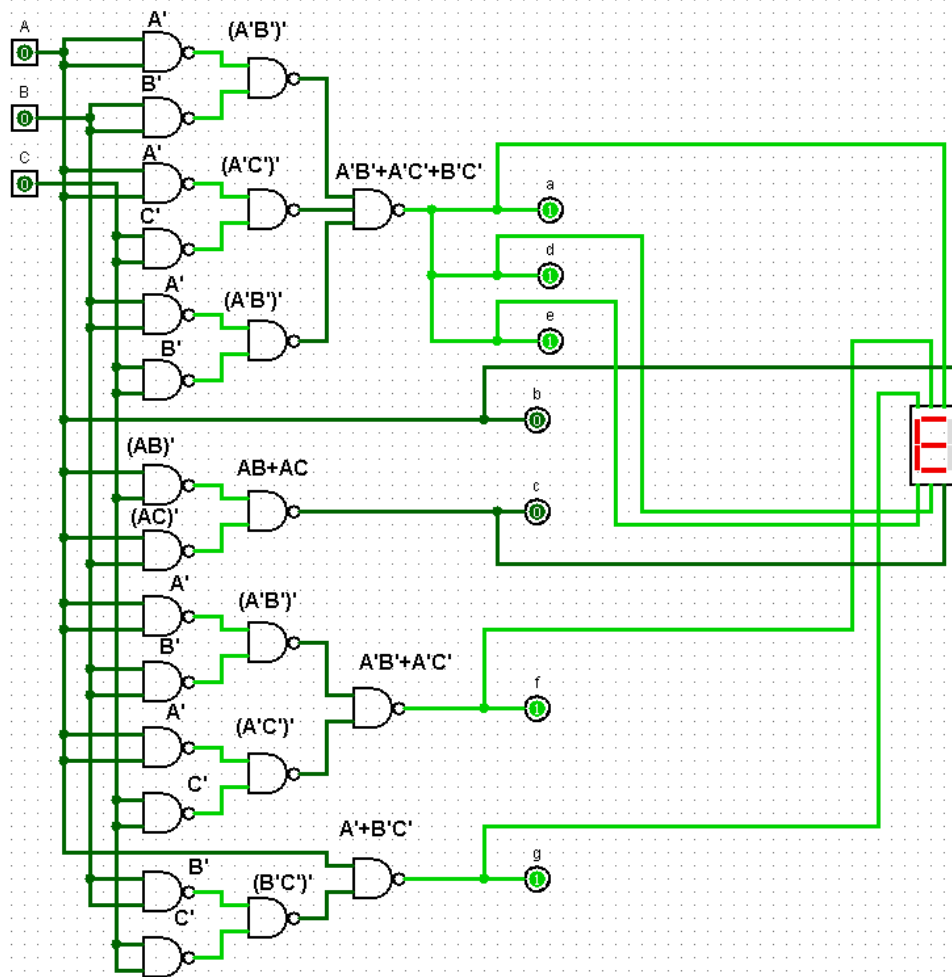

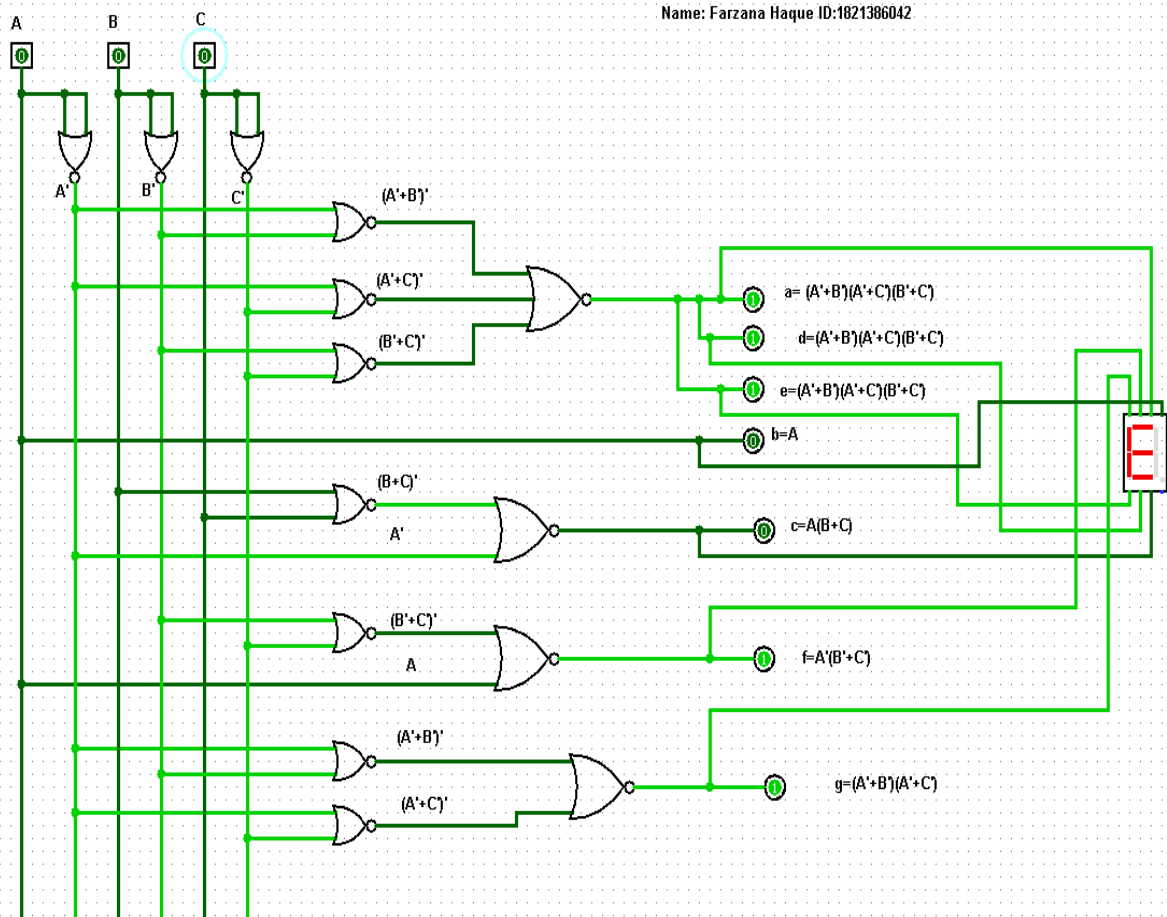□ SOP Circuit implementation with NAND □
□ □ □ □ □



Implementation with NOR